

NOR Gate

The NOR gate.



A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

Output Y is 1 only when no input is 1.