

NOT Gate

The NOT gate.



A	Y
0	1
1	0

Output Y is the inverse of the input.