

OR gate

The OR gate.



A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

Output Y is 1 when at least one input is 1.