

Full Adder

A full adder adds three bits (A, B, cin) and produces Sum and cout.

