

AND Gate

The AND gate.



A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

Output Y is 1 only when all inputs are 1.