

Logic Not Gate



NOT Gate (Inverter)

A	Y
0	1
1	0

Truth Tab